

# ANALOG ELECTRONICS - Project

G.VARSHIT EE19BTECH11020

December 13, 2020

## 1 Active-RC Maximally Flat Low-Pass Filter

### 1.1 Hand calculation

① Given 3 dB Bandwidth,  $\omega_n = 2\pi(1000)\text{Hz} = 2000\pi\text{Hz}$   
also given Rejection  $> 20\text{dB}$  for  $\omega_o > 2\pi(2000)\text{Hz}$

$$20\left(\log\left|\frac{1}{\sqrt{1+\left(\frac{\omega_o}{\omega_n}\right)^{2n}}}\right| - \log\left|\frac{1}{\sqrt{1+\left(\frac{\omega_o}{\omega_n}\right)^{2n}}}\right|\right) > 20$$

$$\therefore \log\left|\frac{\sqrt{1+2^{2n}}}{\sqrt{2}}\right| > 1$$

$$\therefore \left|\frac{\sqrt{1+4^n}}{\sqrt{2}}\right| > 10$$

$$\Rightarrow 1+4^n > 200$$

$$\Rightarrow 4^n > 199$$

$$\Rightarrow \boxed{n \geq 4}$$

We need a 4<sup>th</sup> order system to realise the maximally flat low pass filter

This can be obtained by cascading two second order systems

WK Poles of 4<sup>th</sup> order system are given by

$$S = \omega_n e^{j \frac{2K+1}{2N} \pi + j\pi/2} \quad \text{where } K=0, 1, \dots, N-1$$

here poles are  $s_1 = \omega_n e^{j \frac{5\pi}{8}}$ ,  $s_2 = \omega_n e^{j \frac{7\pi}{8}}$   
 $s_3 = \omega_n e^{j \frac{9\pi}{8}}$ ,  $s_4 = \omega_n e^{j \frac{11\pi}{8}}$

$$s_{1,4} = \omega_n (\cos(5\pi/8) \pm j \sin(5\pi/8)) \quad \text{--- (A)}$$

$$s_{2,3} = \omega_n (\cos(7\pi/8) \pm j \sin(7\pi/8)) \quad \text{--- (B)}$$

$s_{1,4}$  are poles of 1<sup>st</sup> second order filter  $\rightarrow$  Filter 1

$s_{2,3}$  are poles of 2<sup>nd</sup> second order filter  $\rightarrow$  Filter 2

But we know from state-space biquad

$$\frac{V_{out}}{V_{in}} = \frac{R/R_i}{D(s)}$$

where  $D(s) = s^2 + 2s\omega_n \zeta + \omega_n^2$

also  $\boxed{D.c.gain = 0dB} \rightarrow \boxed{R = R_i}$

Poles  $\rightarrow$  Roots of  $D(s) = 0$

$$\rightarrow \boxed{S = \pm \omega_n (-\zeta \pm j\sqrt{1-\zeta^2})} \quad \text{--- (1)}$$

comparing (A), (1)

$$-s_1 = \cos(5\pi/8) \rightarrow \boxed{s_1 = 0.382} \rightarrow \text{Filter (1)}$$

comparing (B), (1)

$$-s_2 = \cos(7\pi/8) \rightarrow \boxed{s_2 = 0.923} \rightarrow \text{Filter (2)}$$

Component values of 1<sup>st</sup> state-space biquad filter

$$\omega_n = 2000\pi \text{ Hz}, \quad \zeta_1 = 0.382$$

$$\therefore \text{we know } \omega_n = \frac{1}{RC} \quad \text{and} \quad 2\zeta_1 \omega_n = \frac{1}{R_0 C}$$

$$\text{let us assume } R = 5 \text{ k}\Omega \Rightarrow C = \frac{1}{5 \times 10^3 \times 2\pi \times 10^3}$$

$$C = 0.0318 \mu\text{F}$$

$$\therefore R_0 = \frac{1}{0.0318 \times 10^{-6} \times 2 \times 0.382 \times 2\pi \times 10^3}$$

$$R_0 = 6.55 \text{ k}\Omega \quad \text{and} \quad R_i = 5 \text{ k}\Omega$$

11<sup>th</sup> component values of 2<sup>nd</sup> state-space biquad filter

$$\omega_n = 2000\pi \text{ Hz}, \quad \zeta_2 = 0.923$$


$$\text{consider } R' = 5 \text{ k}\Omega \Rightarrow C' = \frac{1}{5 \times 10^3 \times 2\pi \times 10^3} = 0.0318 \mu\text{F}$$

$$R_0 = \frac{1}{2 \times 0.923 \times 2\pi \times 10^3 \times 0.0318 \times 10^{-6}} \Rightarrow R_0' = 2.711 \text{ k}\Omega$$


$$R' = R_i' = 5 \text{ k}\Omega$$
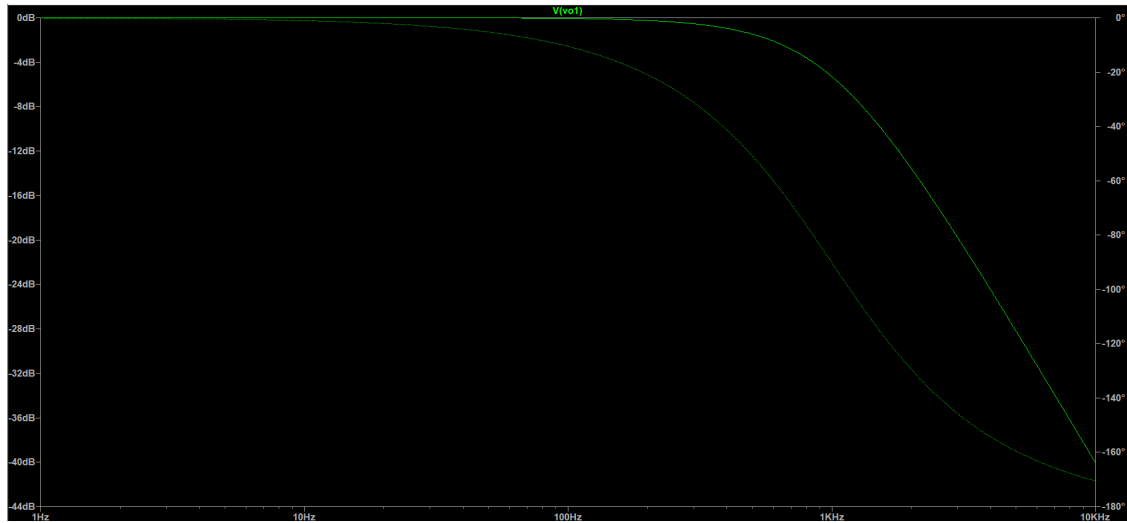
## 1.2 Ordering the filters in the cascade

- As shown in the hand calculations one of the filters has damping factor = 0.923, while the other has damping factor = 0.382.
- So the filter with damping factor of 0.923 ( $> \frac{1}{\sqrt{2}}$ ) shows no peaking.
- Whereas the filter with damping factor of 0.382 ( $< \frac{1}{\sqrt{2}}$ ) shows peaking.
- Hence the filter with damping factor of 0.923 is ordered first in position of cascade, to ensure no peaking at both the output nodes. ( $V_{O1}$  and  $V_{O2}$ )
- Also the output of the cascaded system would be maximally flat response without any peaking.




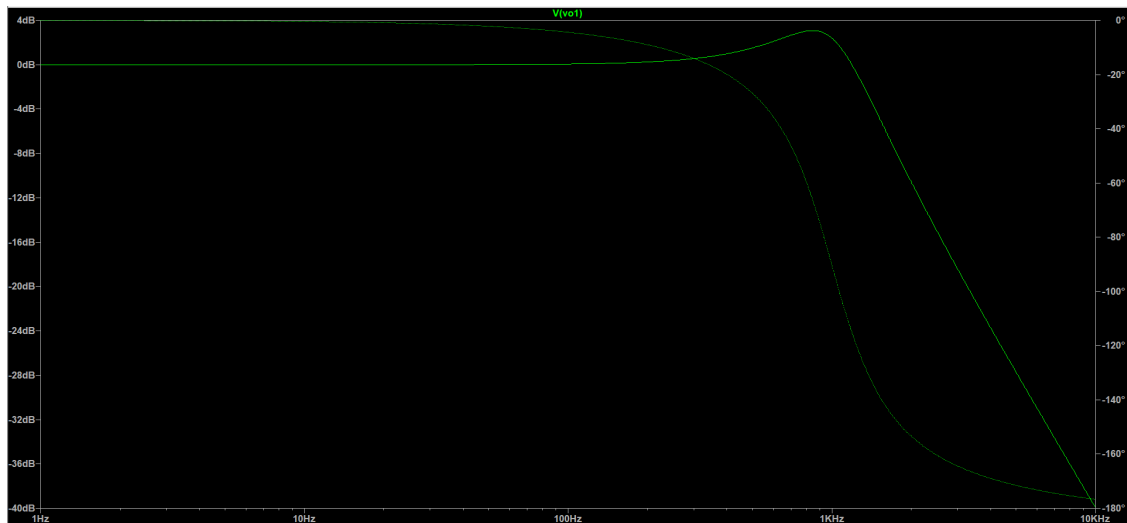Output of filter with damping factor 0.923




Output of filter with damping factor 0.382


### 1.3 Circuit Diagram

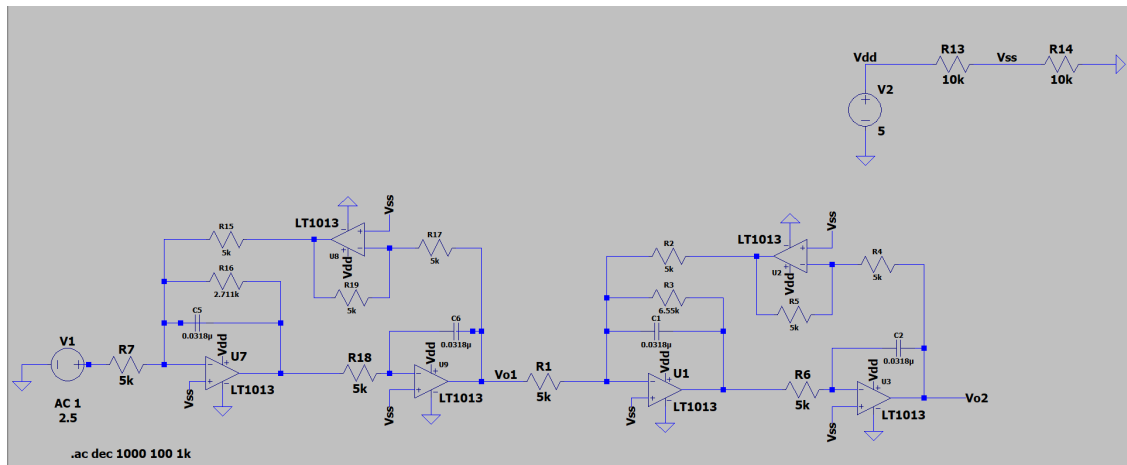

## 1.4 Frequency Response

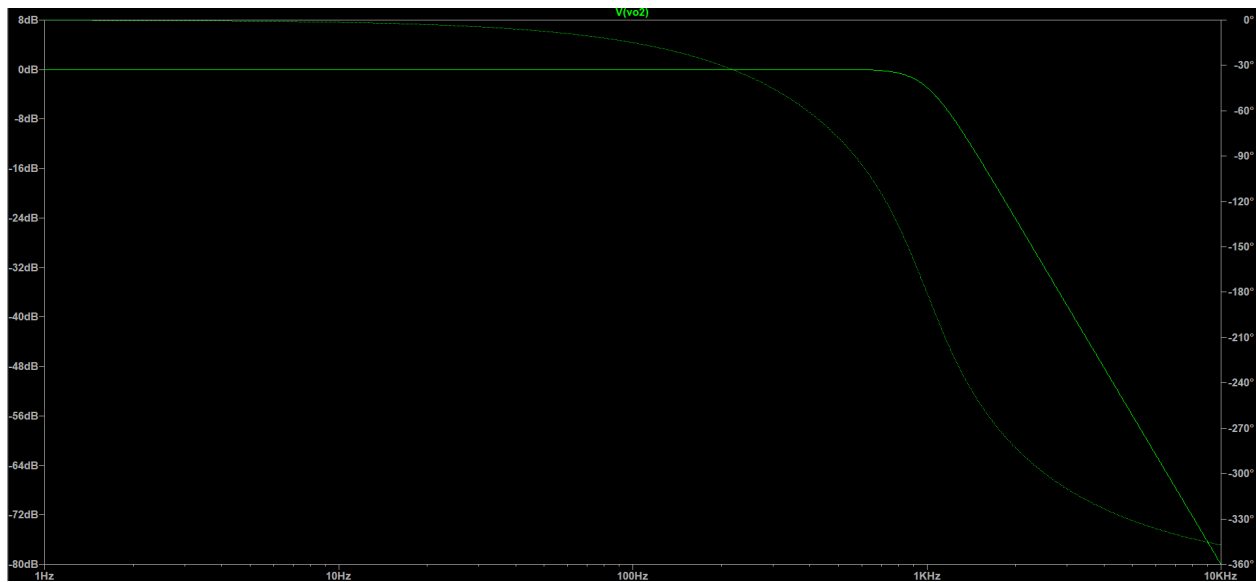

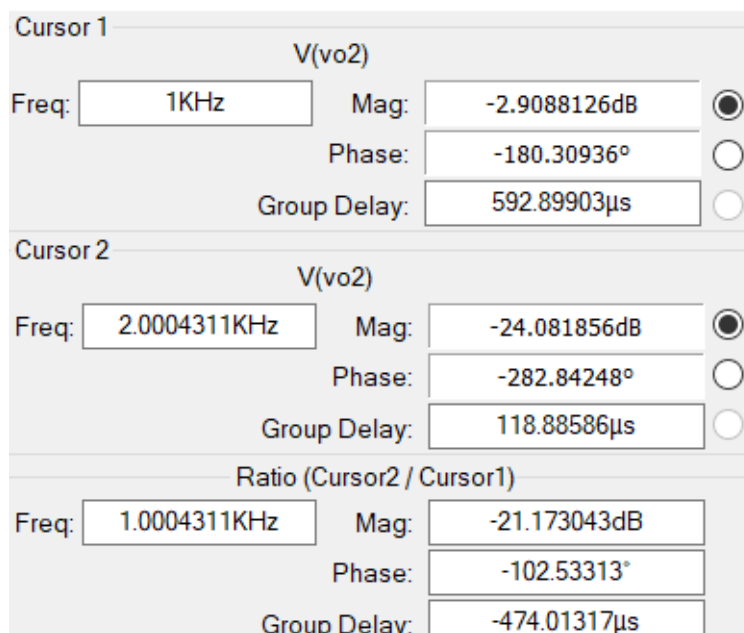
Magnitude and phase frequency response till 10 kHz



Indicating bandwidth and rejection

- We can observe the 3db bandwidth at approximately 1kHz.
- We can also observe the magnitude of around -24db at 2kHz, which implies rejection is greater than 20dB.


## 1.5 Input-output DC characteristics

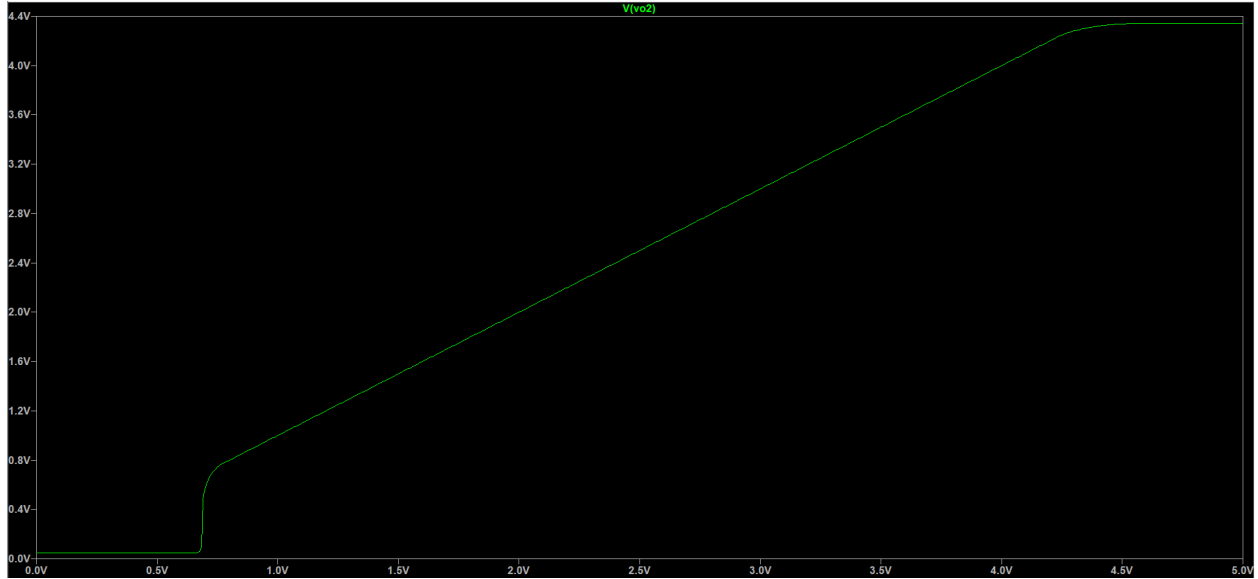

DC characteristics with input varying from 0 V to 5 V.

- We can see that output is constant at 0.145V for a while ( $V_{in} < 0.8V$ ) and then increases suddenly, due to non ideality of Op-amp.
- Later it suddenly increases and becomes equal to input (until 4.4V) , since it is a low pass filter and also the DC gain is zero db.
- Finally it settles at constant value ( $\approx 4.4V$ ), this is because the voltage difference between terminals of Op-amp LT1013 settles at some non-zero constant value.


## 1.6 Magnitude response till 10 MHz

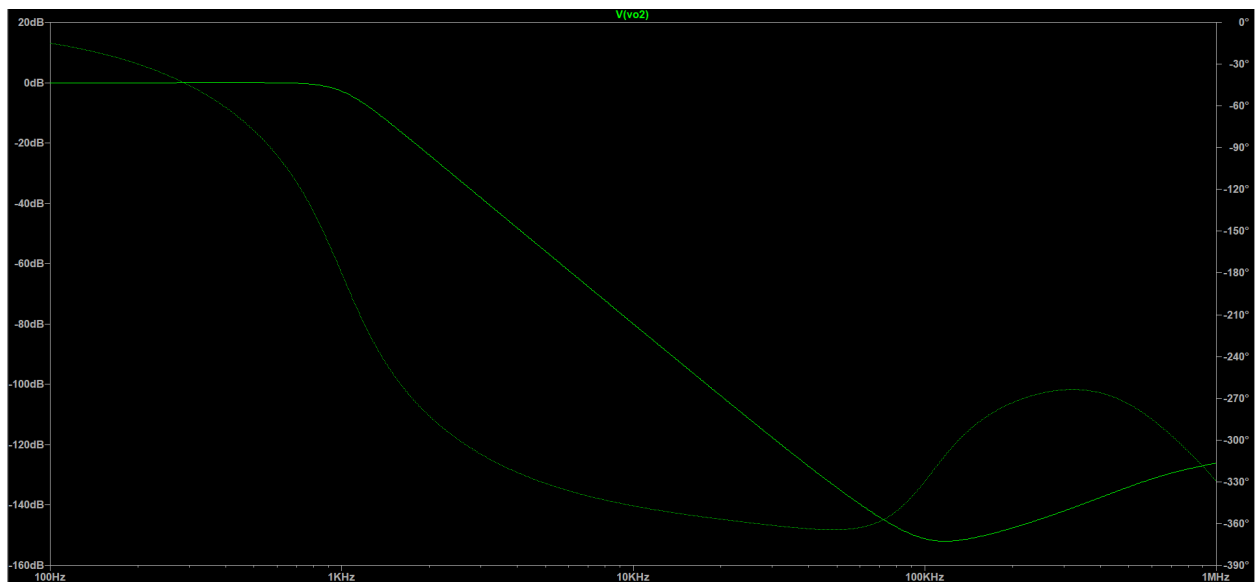

The high frequency behaviour

- We can observe that the above plot is abnormal.
- This is because of non ideal nature of Op-amp LT1013, as it has finite UGB unlike the ideal Op-amp with infinite UGB.

## 1.7 Step response

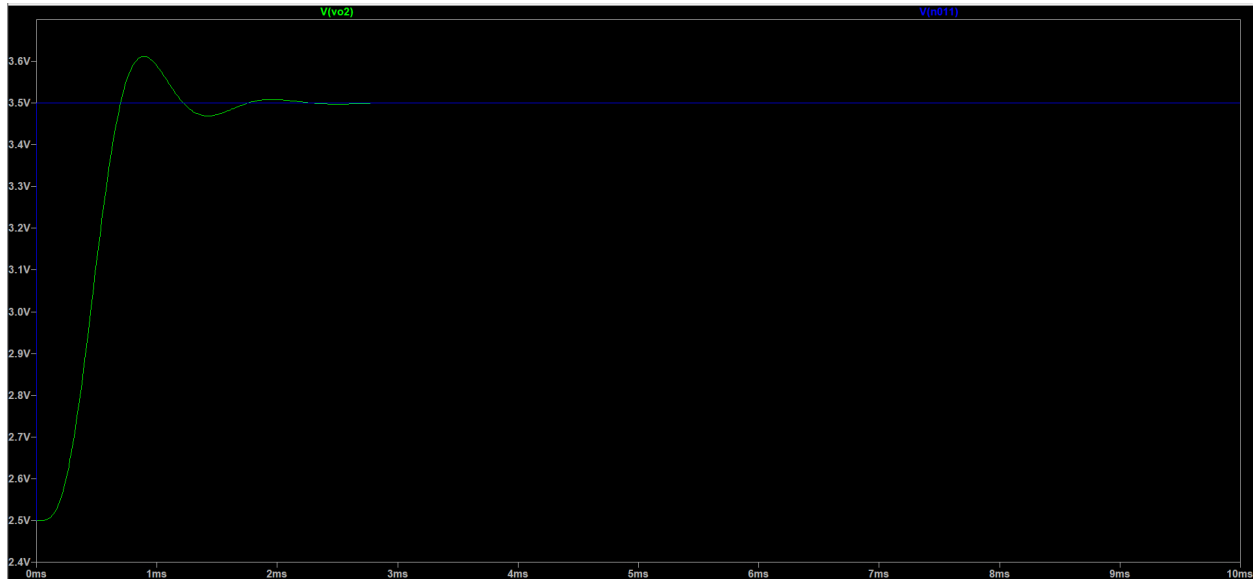

Step response for input going from 2.5 V to 3.5 V in 1 ns

- We can observe output settles to 3.5V at steady state once all the transients die out.
- We can also observe it is a under-damped response because all the poles are complex conjugates.